
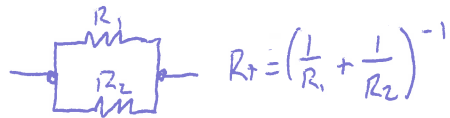



Resistors

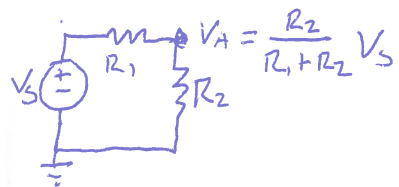

Voltage Divider



Current Divider

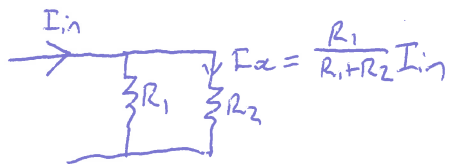

Circuit Equations

Ohm's Law $V = IR$



Power Across Resistor $P = VI = I^2 R = \frac{V^2}{R}$

Inst. Power Inductor $P_L = \frac{1}{2} L I^2$

Inst. Power Capacitor $P_C = \frac{1}{2} C V^2$

INSTANTANEOUS

Zeroing Sources

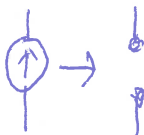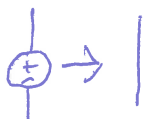

Nodal Analysis

1. Form KCL equations
e.g. $I_1 = I_2 - I_3$

2. Express currents in terms of node voltages

e.g. V_1, I_1, R_1, V_3
 $I_1 = \frac{V_1 - V_3}{R_1}$

3. Sub equations from ② into ①

4. Solve for node voltages


5. Use nodal voltages to find branch currents

6. Check $\sum P = 0$

Equivalent Circuits

Thevenin

Norton

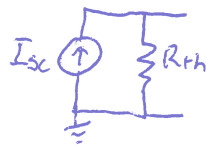

To find V_{oc} :

Leave circuit as-is and find voltage across open ports



Mesh Analysis

1. Draw current loops

2. Form Mesh equation

Hint: look for direction across voltage sources



@ I_x : $V_s = R_1 I_x + (I_x - I_y) R_2 + R_3 I_x$

3. Solve for mesh currents

4. Relate mesh currents to branch currents

5. From ground, calculate node voltages

6. Check $\sum P = 0$

To find I_{sc} :


Short the output only and find current



$$I_{sc} = \frac{R_2}{R_2 + R_3} \left(\frac{V_s}{R_1 + R_2 \parallel R_3} \right)$$

↑
Input current

Sinusoids

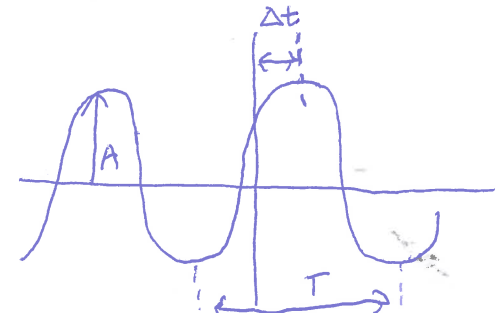

$$V(t) = A \cos(\omega t + \phi)$$

$$f = \frac{1}{T}, \omega = 2\pi f$$


$$\phi = \frac{\Delta t}{T} \times 2\pi$$

Positive phase if wave is left shifted

Negative otherwise

To find R_{th} :

Zero all sources and minimize

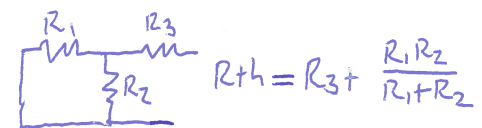

Load Line

